

This question paper contains 4 printed pages]

Roll No.

--	--	--	--	--	--	--	--	--	--	--

S. No. of Question Paper : 1584

Unique Paper Code : 222204 C

Name of the Paper : Digital Electronics (PHHT-206)

Name of the Course : B.Sc. (Hons.) Physics

Semester : II

Duration : 3 Hours

Maximum Marks : 75

(Write your Roll No. on the top immediately on receipt of this question paper.)

Attempt all *five* questions.

1. Attempt any *five* of the following : 5×3=15

- (a) Draw the circuit for 4-bit odd parity generator.
- (b) Define Common Mode Rejection Ratio (CMRR) for an Op-amp.
- (c) Define accuracy and resolution of D/A convertor.
- (d) How many flip-flops are required to produce divide by 64 counters ?
- (e) Define *set up time* and *hold time* in flip-flops.

P.T.O.

(f) Prove that :

$$(A + B)(\bar{A} + C)(B + C) = (A + B)(\bar{A} + C).$$

(g) Subtract 20.25_{10} from 34.75_{10} using 2's complement method.

(h) Draw the circuit diagram of clocked RS FF using NAND gates only.

2. (a) Draw the circuit diagram of Astable multivibrator using IC555 timer and explain its operation. Obtain the expression for frequency of output waveform. Determine the condition under which 50% duty cycle is possible. 7½

(b) For a 4-bit R-2R ladder D/A converter the input levels are logic 0 = 0 V and logic 1 = +10 V, find the :

(i) Output voltage caused by each bit.

(ii) Full scale output voltage of a ladder.

(iii) Percentage resolution. 7½

Or

Draw the block diagram of CRO. Explain the function of :

(i) Time base generator

(ii) Delay line

(iii) Aquadag Coating. 7½

3. (a) What is the difference between open loop and closed loop gain of an op-amp ? Plot transfer characteristics of inverting Amplifier of gain of 10 if Op-Amp is given dual power supply of ± 12 volts. 7½

- (b) Using Operational Amplifier, design a circuit for performing the following operation :

$$V_0 = -(V_1 + 4V_2 + 2V_3)$$

where V_0 is the output voltage; V_1 , V_2 and V_3 are the input voltages. 7½

Or

Describe how an operational amplifier is used to perform the mathematical operation of differentiation. What would be the expression for output if the input is given by :

$$V_{in} = V \sin \omega t. \quad \text{7½}$$

4. (a) Minimize the following logic function using K-map :

$$F(A, B, C, D) = \Sigma(0, 4, 7, 8, 10, 13, 15) + \Sigma d(2, 5, 12).$$

Write the minimized Boolean expression in sum of product form and realize it using 2-input NAND gates only. 7½

- (b) What is a multiplexer ? Implement the following function with 8×1 multiplexer :

$$F(A, B, C, D) = \Sigma(0, 1, 2, 3, 4, 8, 11, 14, 15). \quad \text{7½}$$

Or

What is a decoder ? Design a full adder circuit using a decoder and OR gates. 7½

P.T.O.

5. (a) Draw the circuit diagram of JK-FF using NAND gates and give its truth table. How JK flip-flop can be converted to D flip-flop and T flip-flop ? Explain with relevant block diagram ? Give *one* application of each of D flip-flop and T flip-flop. 7½
- (b) Design a MOD-6 synchronous counter using block diagram of appropriate flip-flops. 7½

Or

Draw the circuit diagram of 4-bit bi-directional shift register. Explain its operation. 7½