

[This question paper contains 5 printed pages.]

6589

Your Roll No.

B.Sc. (Hons.) Computer Science / I Sem. B

Paper – CS 104 : DIGITAL ELECTRONICS

(Admissions of 2001 to 2009)

Time : 3 Hours

Maximum Marks : 75

*(Write your Roll No. on the top immediately
on receipt of this question paper.)*

Attempt all questions.

Parts of a question must be answered together.

1. (a) Show the bit configuration of a 24-cell register when it's content represents the decimal number 295 in BCD. (1)
- (b) Subtract $(10110.011)_2$ from $(11010.1)_2$ and verify the result by showing equivalent decimal subtraction. (2)
- (c) What is a gray code? (1)
2. (a) Show the dual of the exclusive – OR is equal to it's complement. (3)
- (b) A majority gate is a digital circuit whose output is equal to 1 if the majority of the inputs are 1s. The

P.T.O.

output is 0 otherwise. By means of a truth table, find the boolean function implemented by a 3-input majority gate. Simplify the function. (4)

- (c) What is the usage of a buffer in a circuit? (1)
- (d) Simplify the boolean function given below by means of tabulation method.

$$F(A, B, C, D, E, F, G) = \Sigma(20, 28, 38, 39, 52, 60, 102, 103, 127)$$

(5)

3. (a) Design a circuit that detects an error in the representation of a decimal digit in BCD. In other words, obtain a logic diagram whose output is logic 1 when the inputs contain an unused combination in the code. (4)

- (b) Using 4 exclusive - OR gates and a 4-bit full adders MSI circuit, construct 4-bit parallel adder/subtractor. Use an input select variable 'V' so that when $V = 0$, the circuit adds and when $V = 1$, the circuit subtracts. (Hint: use 2's complement subtraction). (5)


- (c) Design a circuit specified by 3 functions given below with a dual 4-line to 1-line multiplexer, an OR gate and an inverter

$$\begin{aligned} F_1 &= x'y' + xyz' \\ F_2 &= x' + y \\ F_3 &= xy + x'y' \end{aligned}$$

(4)

4. (a) A flip flop has a 20 nsec delay from the time it's clock pulse input goes from 1 to 0 to the time the output is complemented. What is the maximum delay in a 10-bit binary ripple counter that uses these flip flops? What is the maximum frequency that the counter can operate at reliability? (2)

 - (b) The full adder of given figure receives two external inputs x and y . The third input z comes from the output of a D flip flop. The carry output is transferred to the flip flop every clock pulse. The external output 'S' gives the sum x , y and z . Obtain the State Table and State Diagram of the sequential circuit (4)



- (c) Design a BCD counter with JK flip flop. (6)

5. (a) Design a shift register with parallel load that operates according to the following table :

Shift	Load	Operation
0	0	No Change
0	1	Load 11 Data
1	X	Right Shift

(6)

- (b) If the data at sender site is 1101, but received as 0101 at the receiver site, using Hamming code method show that bit no. 3 is in error. (5)
6. (a) Consider a sequential system that records (counts) the occurrence of 55 different events (numbered from 1 to 55), which take place one at a time. When the count of event i becomes a multiple of 100, the output $z(t) = i$, otherwise $z(t) = 0$. Obtain a state description of the system. (6)
- (b) Determine the minimal state table equivalent to the following state table : (5)

Present State	Input			
	$x = a$	$x = b$	$x = c$	$x = d$
A	E, 1	C, 0	B, 1	E, 1
B	C, 0	F, 1	E, 1	B, 0
C	B, 1	A, 0	D, 1	F, 1
D	G, 0	F, 1	E, 1	B, 0
E	C, 0	F, 1	D, 1	E, 0
F	C, 1	F, 1	D, 0	H, 0
G	D, 1	A, 0	B, 1	F, 1
H	B, 1	C, 0	E, 1	F, 1

NS, z

7. (a) How many address inputs, data inputs and data outputs are required for $16K \times 12$ memory. (3)

(b) An asynchronous sequential circuit is described by the following excitation and output functions

$$Y = X_1 X_2' + (X_1 + X_2')Y$$

$$Z = Y$$

(i) Derive the Transition table

(ii) Derive the Output map

(iii) Obtain the 2 state flow table (3)

(c) Using T flip flops, design a modulo-5 counter whose specification is :

Input : $x(t) \in \{0, 1\}$

Output : $z(t) \in \{0, 1, 2, 3, 4\}$

State : $s(t) \in \{S_0, S_1, S_2, S_3, S_4\}$

Initial state : $s(0) = S_0$

function : as specified by the following State Diagram (5)

